

#### **Electrical Power and Machines Engineering Department**



**Faculty of Engineering** 

# ELECTRICAL POWER SYSTEM (1) EXPERIMENTS FOR 2<sup>ND</sup> YEAR STUDENT 2017

**Eng. Eman Gaber** 


**Eng. Mohamed Elkadeem** 


**Eng. Mahmoud Elkazaz** 

Eng. Abd El-Aziz Gebril


#### **CONTENTS**

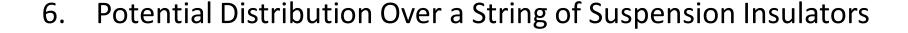- 1. Performance of short transmission lines
- 2. Determination of short transmission line model constants
- 3. Performance of Medium Transmission Lines (T-Model)
- 4. Performance of Medium Transmission Lines ( $\pi$ -Model)
- 5. Determination of the Dc Distributor Performance



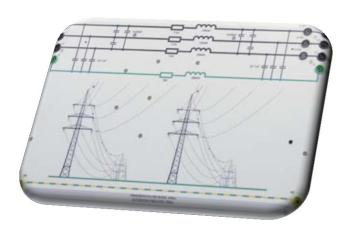

## **OUTLINES**

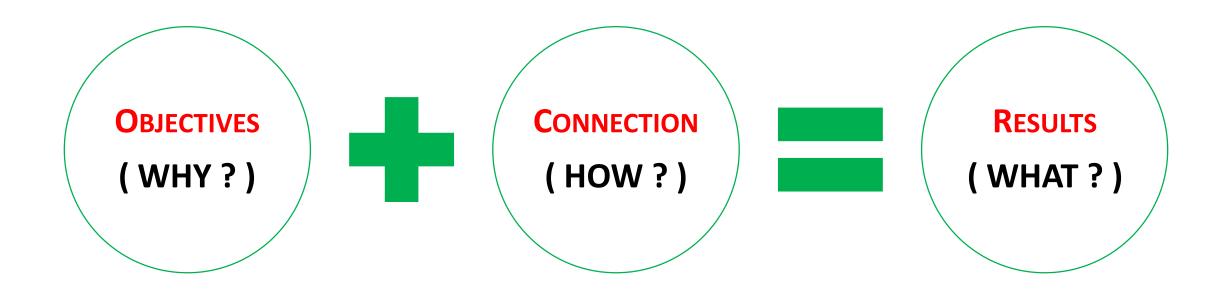

# **EXP (2)**

# Determination of short transmission line model constants (A, B, C & D)


### **OBJECTIVES**

To determine experimentally the magnitude and angle of each of the four **general constants of a TL** 

$$V_{s} = AV_{r} + BI_{r}$$

$$I_s = CV_r + DI_r$$

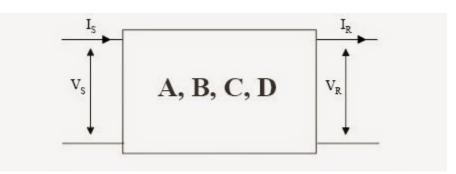
 <u>Two port network</u>: used for simplify the performance analysis of any type of transmission lines.



 Useful in designing and simulating power system networks.

# **CONNECTION DIAGRAM**


#### Open Circuit test

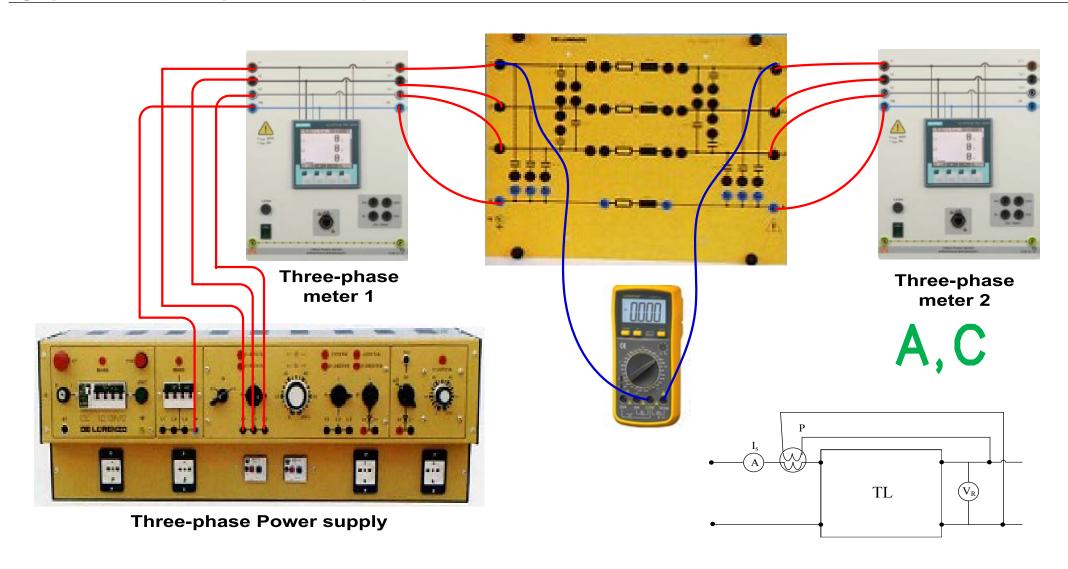

## **CONNECTION DIAGRAM**


#### Open Circuit test

$$A = \left| \frac{V_s}{V_r} \right|$$

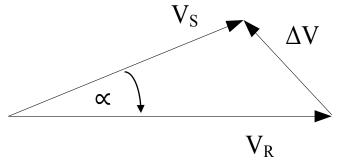


$$|C| = \left| \frac{I_s}{V_r} \right|$$

$$\alpha = \cos^{-1} \left| \frac{P}{V_r I_s} \right|$$

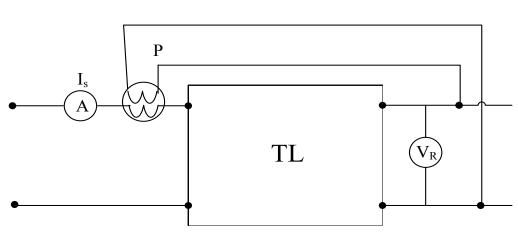

## **CONNECTION DIAGRAM**

#### Short Circuit test

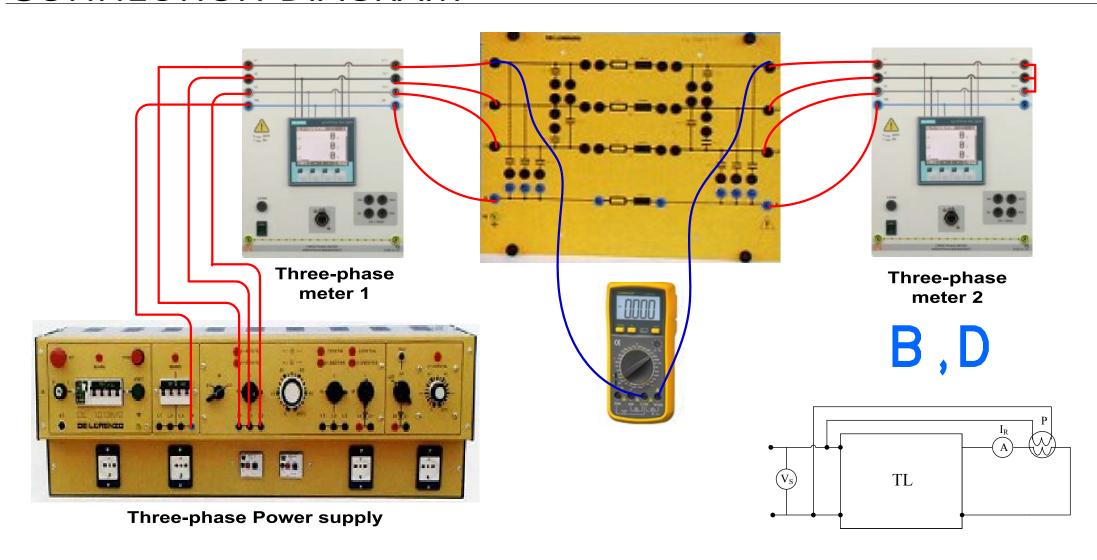


# **RESULTS**

A	B (ohm)	C (mho)	D
?	?	?	?



$$B = \left| \frac{V_s}{I_r} \right| \qquad \beta = \cos^{-1} \left| \frac{P}{V_s I_r} \right|$$

$$AD-BC=1$$

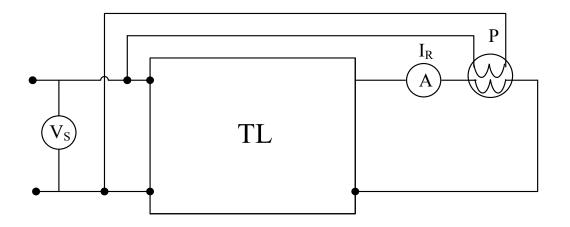

#### **DISCUSSION**

- 1. Illustrate with connection diagram how you can determine the overhead transmission line constants?
- 2. Write down the relationships among transmission line constants.

http://www.electrical4u.com/abcd-parameters-of-transmission-line/

# EXP.2 RESULTS

#### • OC TEST

Vs	Ir	Is	Vr	Pr	Ps	$\Delta V$
V	mA	mA	V	W	W	$oldsymbol{V}$
94	0.00	0.00	100	0.00	0.00	14

#### • SC TEST

Vs	Ir	Is	Vr	Pr	Ps	$\Delta V$
V	mA	mA	V	W	W	$oldsymbol{V}$
32	340	340	0.00	0.00	2.00	-

#### **RESULTS**

## What do the measurement results indicate?!



# **THANKS**